

Name: V. Sajeevan.

Index Number: 160544C

Practical Date: 02.11.2017

Submission Date: 09.11.2017

Subject: CS 2052 Computer Architecture

REPORT ON LAB 7

7- SEGMENT DISPLAY


Lab Task:

- Creating a symbol for 4-bit Arithmetic unit
- Complete the table of inputs and outputs.
- Design and Develop a 7-segment display using the output from lookup table
- Verification of its functionality via simulation and on the BASYS2 development board.

Lookup table:

Output from RCA					Segments to Switch On						
s3	s2	s1	s0	Hex.Value	A	B	C	D	E	F	G
0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	1	0	0	1	1	1	1
0	0	1	0	2	0	0	1	0	0	1	0
0	0	1	1	3	0	0	0	0	1	1	0
0	1	0	0	4	1	0	0	1	1	0	0
0	1	0	1	5	0	1	0	0	1	0	0
0	1	1	0	6	0	1	0	0	0	0	0
0	1	1	1	7	0	0	0	1	1	1	1
1	0	0	0	8	0	0	0	0	0	0	0
1	0	0	1	9	0	0	0	0	1	0	0
1	0	1	0	a	0	0	0	1	0	0	0
1	0	1	1	b	1	1	0	0	0	0	0
1	1	0	0	c	0	1	1	0	0	0	1
1	1	0	1	d	1	0	0	0	0	1	0
1	1	1	0	e	0	1	1	0	0	0	0
1	1	1	1	f	0	1	1	1	0	0	0
Hexadecimal value of each column					2812	D860	D004	8492	02BA	208E	1083

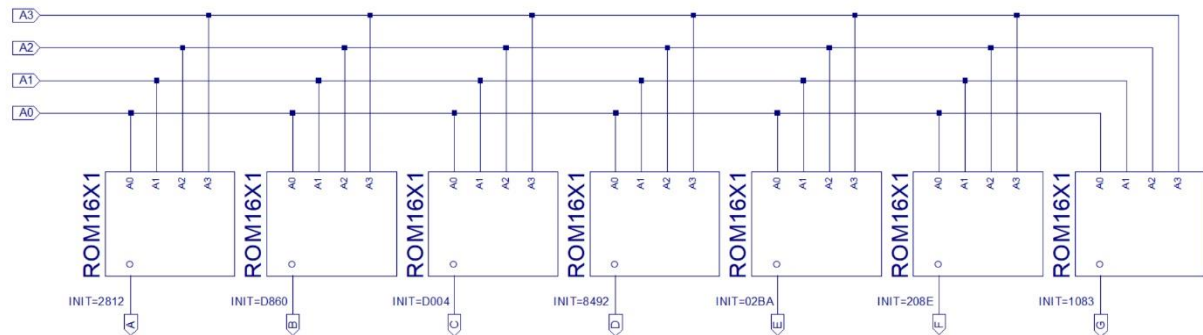Schematic circuit diagram according to the lookup table:




Simulation timing diagram:

The inputs were given regarding the index number.


Index number: 160544C

Binary equivalent: 0b10 0111 0011 0010 0000

Inputs: 0000, 0010, 0011, 0111

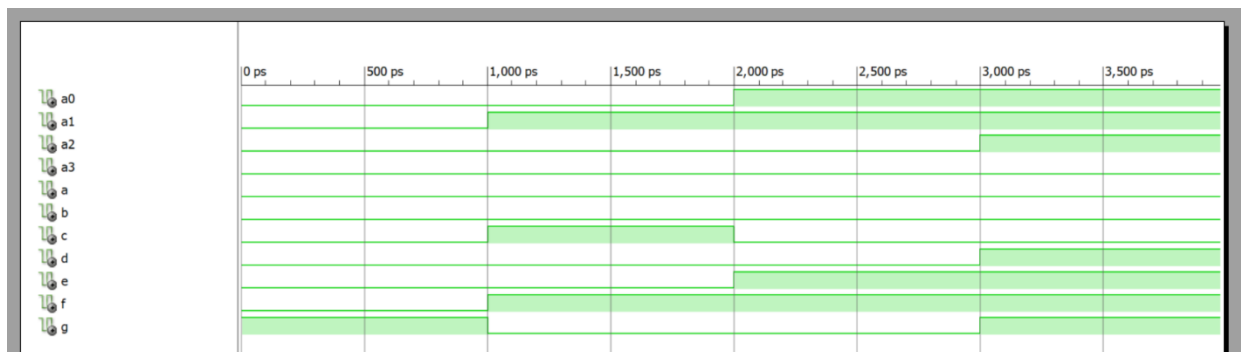

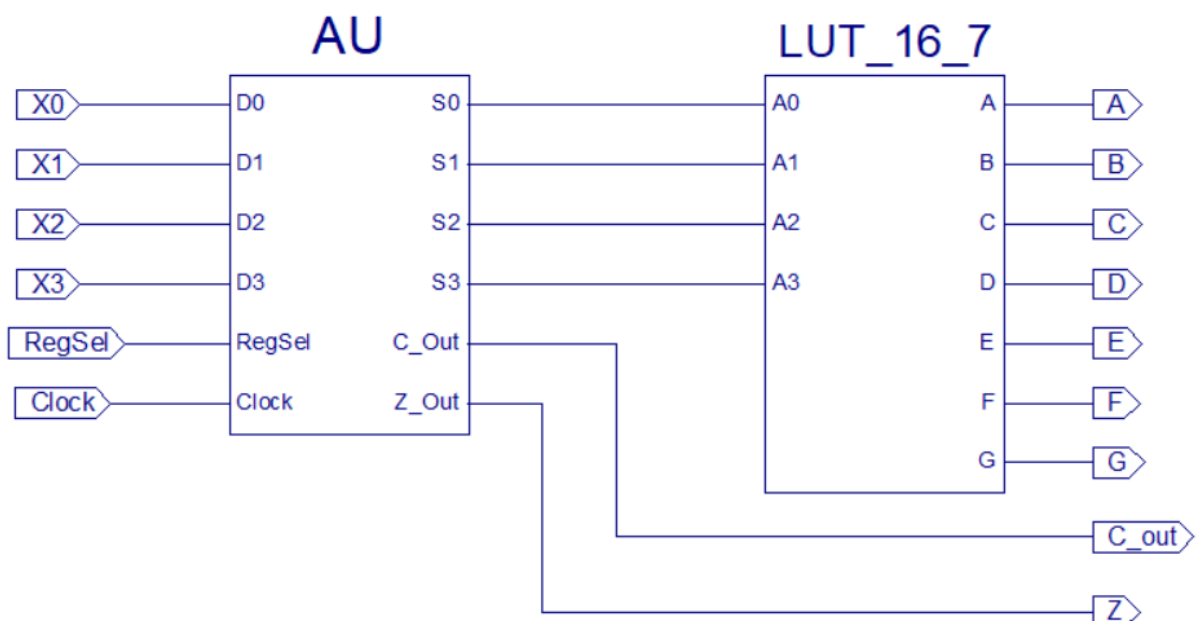Schematic circuit diagram for 7-segmented display:



Discussion:

For each 7-segment, there are 4 common anode terminals. We need to disable three anodes to display only one 7-segment. As the output must be displayed by the right most 7-segment, not gates are connected to the other three anodes.

Conclusion:

At the end of the lab, I was able to

- Design and develop a lookup table using Read Only Memory (ROM).
- Design and develop a 7-segment display using the output from the lookup table.
- Verify their functionality via simulation.
- Verify the functionality of them on the development board.