

Name: V. Sajeevan.

Index Number: 160544C

Practical Date: 07.09.2017

Submission Date: 14.09.2017

REPORT ON LAB 3

RIPPLE CARRY ADDER

Lab Task:

- Finding the Boolean expression for Half Adder (HA) and Full Adder (FA) and simplifying them by using the truth table.
- Building an HA circuit using basic logic gates, simulating it and creating an HA symbol.
- Building an FA circuit using HAs and basic logic gates, simulating it and creating an FA symbol.
- Building a 4-bit Ripple Carry Adder (RCA) using FAs, simulating it and testing on BASYS2.

Half Adder


Truth table and Boolean expression:

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = AB$$

Schematic Circuit:

 


Test bench code:

```
-- *** Test Bench - User Defined Section ***
tb : PROCESS
BEGIN
    -- Make sure to set initial values for A & B
    A <= '0';
    B <= '0';

    -- Repeat signals to form waveform
    AB_LOOP: LOOP
        WAIT FOR 1 ns;
        A <= NOT A;
        WAIT FOR 1 ns;
        B <= NOT B;
        A <= NOT A;
    END LOOP AB_LOOP;
    WAIT; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***
END;
```

Timing diagram:

 

Full Adder

Truth Table:


A	B	C_in	S	C_out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Boolean Expressions:

$$\begin{aligned} S &= \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in} \\ &= \bar{A} (\bar{B} C_{in} + B \bar{C}_{in}) + A (\bar{B} \bar{C}_{in} + B C_{in}) \\ &= \bar{A} (B \oplus C_{in}) + A (\overline{B \oplus C_{in}}) \\ &= A \oplus B \oplus C_{in} \end{aligned}$$

$$\begin{aligned} C_{out} &= \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in} \\ &= (\bar{A} B + A \bar{B}) C_{in} + A B (\bar{C}_{in} + C_{in}) \\ &= (A \oplus B) C_{in} + A B \end{aligned}$$

Schematic Circuit:

 


Test bench code:

```
-- *** Test Bench - User Defined Section ***
tb : PROCESS
BEGIN
    -- Make sure to set initial values for A & B
    A <= '0';
    B <= '0';
    C_in <= '0';
    -- Repeat signals to form waveform
    ABC_LOOP: LOOP
        WAIT FOR 1 ns;
        A <= NOT A;
        WAIT FOR 1 ns;
        B <= NOT B;
        A <= NOT A;
        WAIT FOR 1 ns;
        A <= NOT A;
        WAIT FOR 1 ns;
        C_in <= NOT C_in;
        B <= NOT B;
        A <= NOT A;
    END LOOP ABC_LOOP;
    WAIT; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***


END;
```

Timing diagram:

 

4-bit Ripple Carry Adder:

Schematic Circuit:

 

Test bench code:

```
-- INDEX NO. 160544C = 0b10 0111 0011 0010 0000
-- *** Test Bench - User Defined Section ***
tb : PROCESS
BEGIN
    C0 <= '0';
    -- Make sure to set initial values for Index No.
    A0 <= '0';
    A1 <= '0';
    A2 <= '0';
    A3 <= '0';
    B0 <= '0';
    B1 <= '1';
    B2 <= '0';
    B3 <= '0';
    WAIT FOR 1 ns;
    A0 <= '1';
    A1 <= '1';
    A2 <= '0';
    A3 <= '0';
    B0 <= '1';
    B1 <= '1';
    B2 <= '1';
    B3 <= '0';
    WAIT FOR 1 ns;
    --Also try 0101 + 1011 and 0111 + 1111
    A0 <= '1';
    A1 <= '0';
    A2 <= '1';
    A3 <= '0';
    B0 <= '1';
    B1 <= '1';
    B2 <= '0';
    B3 <= '1';
    WAIT FOR 1 ns;
    A0 <= '1';
    A1 <= '1';
    A2 <= '1';
    A3 <= '0';
    B0 <= '1';
    B1 <= '1';
    B2 <= '1';
    B3 <= '1';

    --Any 4 other unique combinations
    WAIT FOR 1 ns; -- 0101 + 1011
    A0 <= '1';
    A1 <= '0';
    A2 <= '1';
    A3 <= '0';
    B0 <= '1';
    B1 <= '1';
    B2 <= '0';
    B3 <= '1';
    WAIT FOR 1 ns; -- 0110 + 0101
    A0 <= '0';
    A1 <= '1';
    A2 <= '1';
    A3 <= '0';
    B0 <= '1';
    B1 <= '0';
    B2 <= '1';
    B3 <= '0';
    WAIT FOR 1 ns; -- 1010 + 1001
    A0 <= '0';
    A1 <= '1';
    A2 <= '0';
    A3 <= '1';
    B0 <= '1';
    B1 <= '0';
    B2 <= '0';
    B3 <= '1';
    WAIT FOR 1 ns; --0001 + 1011
    A0 <= '1';
    A1 <= '0';
    A2 <= '0';
    A3 <= '0';
    B0 <= '1';
    B1 <= '1';
    B2 <= '0';
    B3 <= '1';

    WAIT; -- will wait forever
END PROCESS;
-- *** End Test Bench - User Defined Section ***
END;
```

$$160544_{10} = 10\ 0111\ 0011\ 0010\ 0000_2$$

Two sets of inputs were taken from the binary value of index number.


- $0000_2 + 0010_2$
- $0011_2 + 0111_2$

I also try $0101_2 + 1011_2$ and $0111_2 + 1111_2$

Any 4 other unique combinations

- $0101_2 + 1011_2$
- $0110_2 + 0101_2$
- $1010_2 + 1001_2$
- $0001_2 + 1011_2$

Timing diagram:

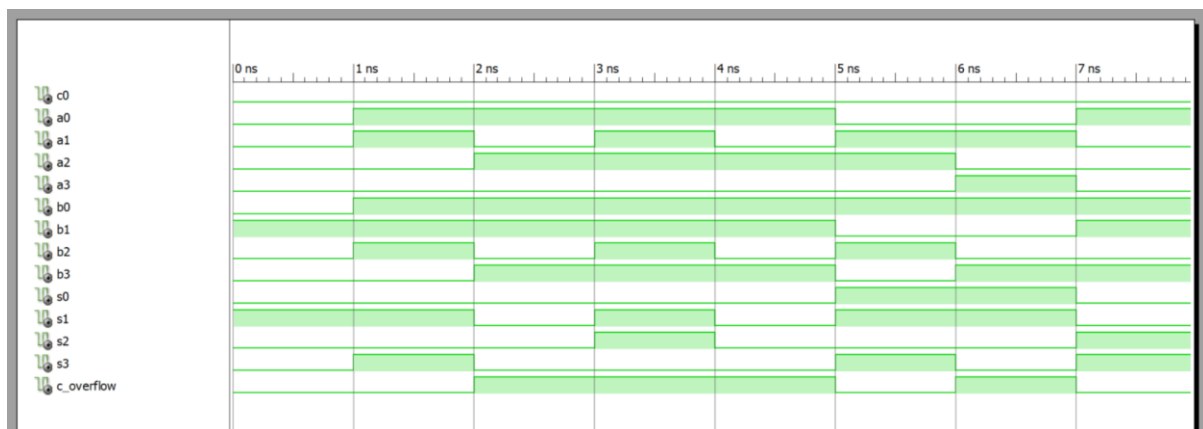

Discussion:

Although we input 4-bit inputs, the outputs may be of more than 4 bits. For example, if we input 1100 and 1011, the output will be 10111. So, we need 5 LEDs to represent this type of outputs. But in our case, LED LD0-LD3 are only considered. So, it is impossible to represent the outputs which are more than 4 bits.

Conclusion:

After finishing the lab, I am able to,

- Design and develop a Half Adder, Full Adder and a Ripple Carry Adder.
- Build more complex components by using the basic components.
- Verify the functionality of them via stimulation and using the development board.