

Group Members: - 1.160400H - K.Mathivathanan

2.160544C – V.Sajeevan

3.160658E – C.Vivek Vinushanth

Module: CS2052 - Computer Architecture

Report: Labs 9-10(Nano-Processor)

Report on Nano Processor


➤ Lab Task:

In both labs, we are assigned to design a simple Nano processor which can execute simple set of instructions. We also should design a 4-bit register bank which contains eight registers and a four-bit processor which can execute minimum four instructions. To complete the task successfully we built,


- Half Adder, Full Adder:
These are one of the basic components in the circuit
- 4 bit add/subtract unit
This unit can add and subtract numbers represented using 2's complement.
- 3-bit adder:
This unit is to increment the program counter.
- 3-bit program counter (PC):
Program counter need to be reset to 0 when required. Hence build it was built using D flip flops with clear as an input. FDC is used to design the program counter and register bank.
- K- way b –bit multiplexers:
A k-way b-bit multiplexer can take 'k' number of inputs, each with b-bits, rather than a single bit, and output is a group of b-bits. There are $\log_2 k$ control bits, and these control bits are used to enable one of the k groups of b bits.
 - ✓ Built a 2-way 3-bit multiplexer.
 - ✓ Built a 2-way 4-bit multiplexer.
 - Built a 8-way 4-bit multiplexer.
- Register:
Can load data from a larger memory into registers where it is used for arithmetic operations and is manipulated or tested by [machine instructions](#). Manipulated data is then often stored back to main memory, either by the same instruction or by a subsequent one. D flipflops have been used as a way of store memory.
- ROM
- Instruction Decoder

✓ **Schematic Diagrams and relevant Simulation diagrams**


➤ **Half Adder:**

 


➤ **Full Adder:**

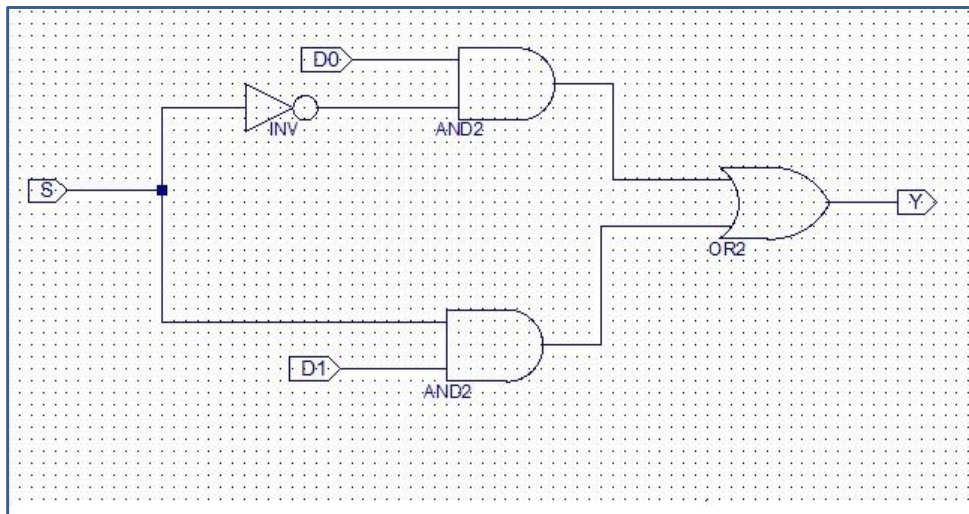


➤ 2 way- 3 bit Mux:

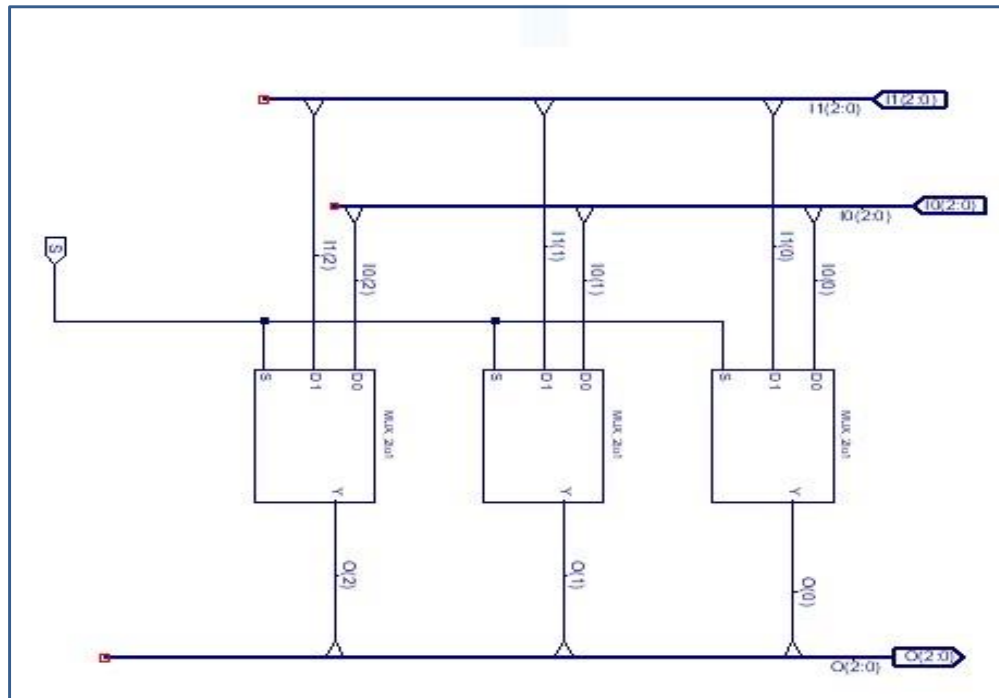


➤ 2 way_4 bit Mux:

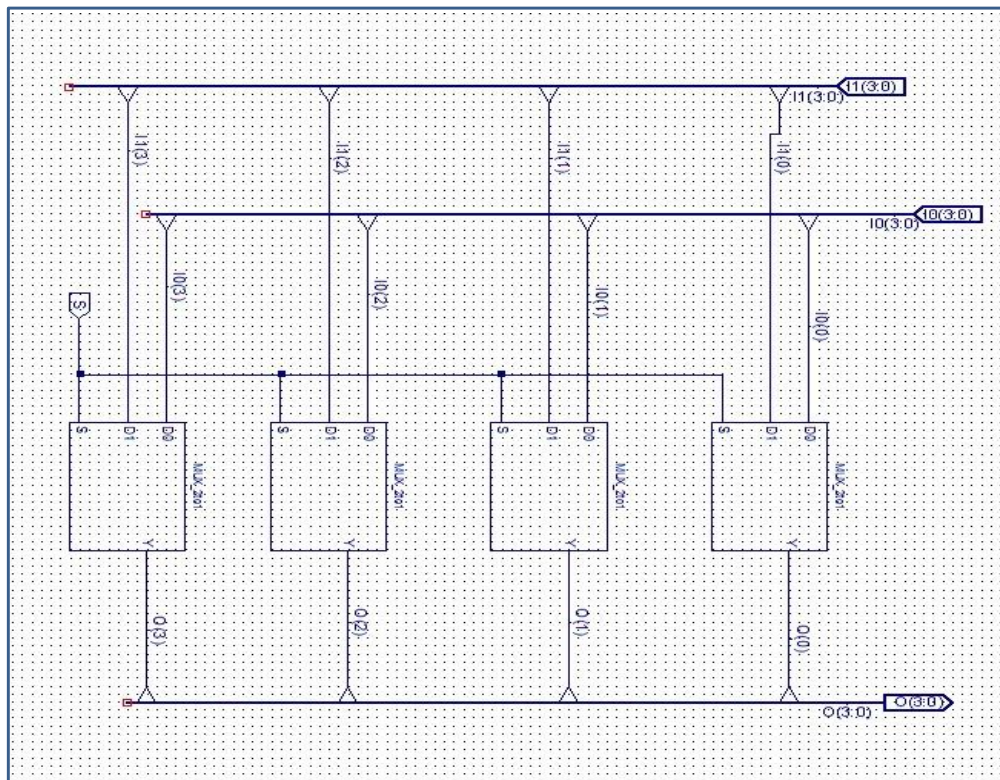

 
❖ Timing diagram for 2-way_4 bit Mux is as follows:




➤ 8 way_1 bit Mux:

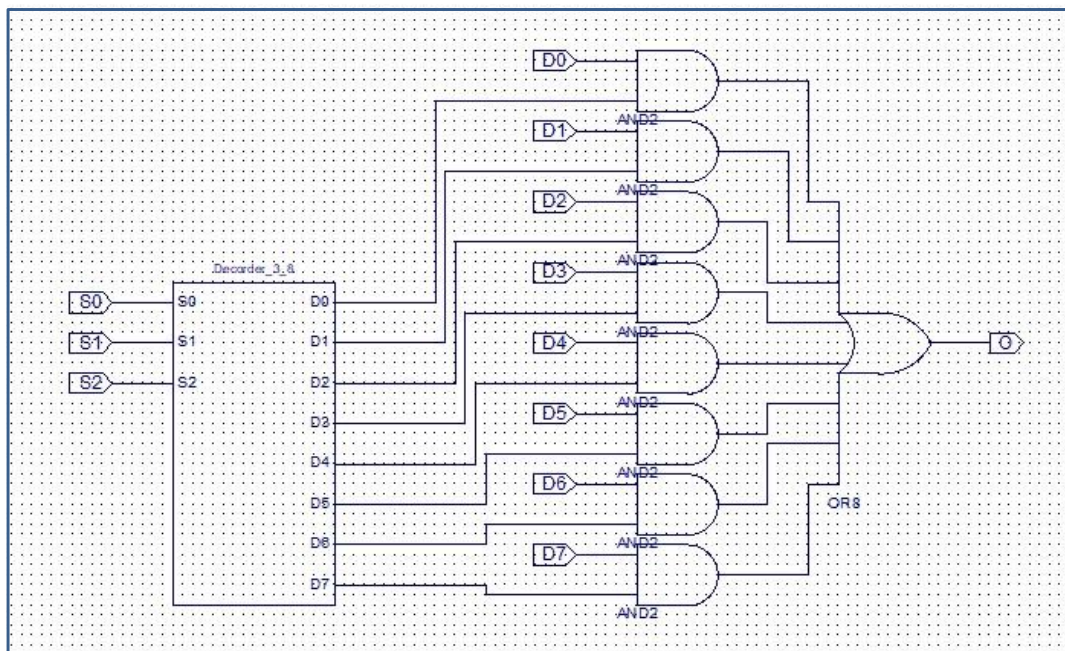


➤ 3 bit-Adder:

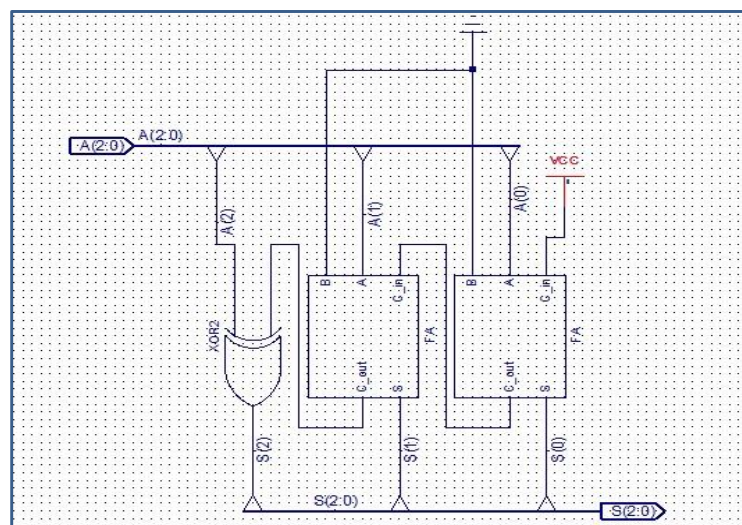

❖ Timing diagram for 3-bit adder:

 


➤ 3_to_8 decoder:

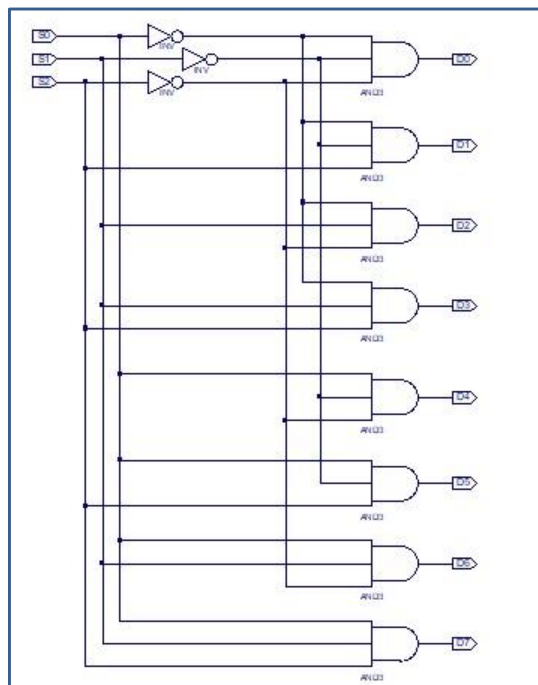


➤ 4_bit_Add/Sub Unit :


✓ Timing diagram is as follows-

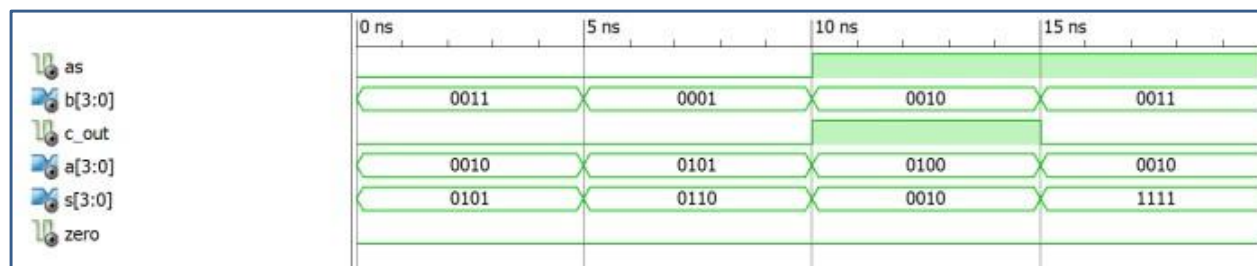


- Schematic of Add/Sub unit:

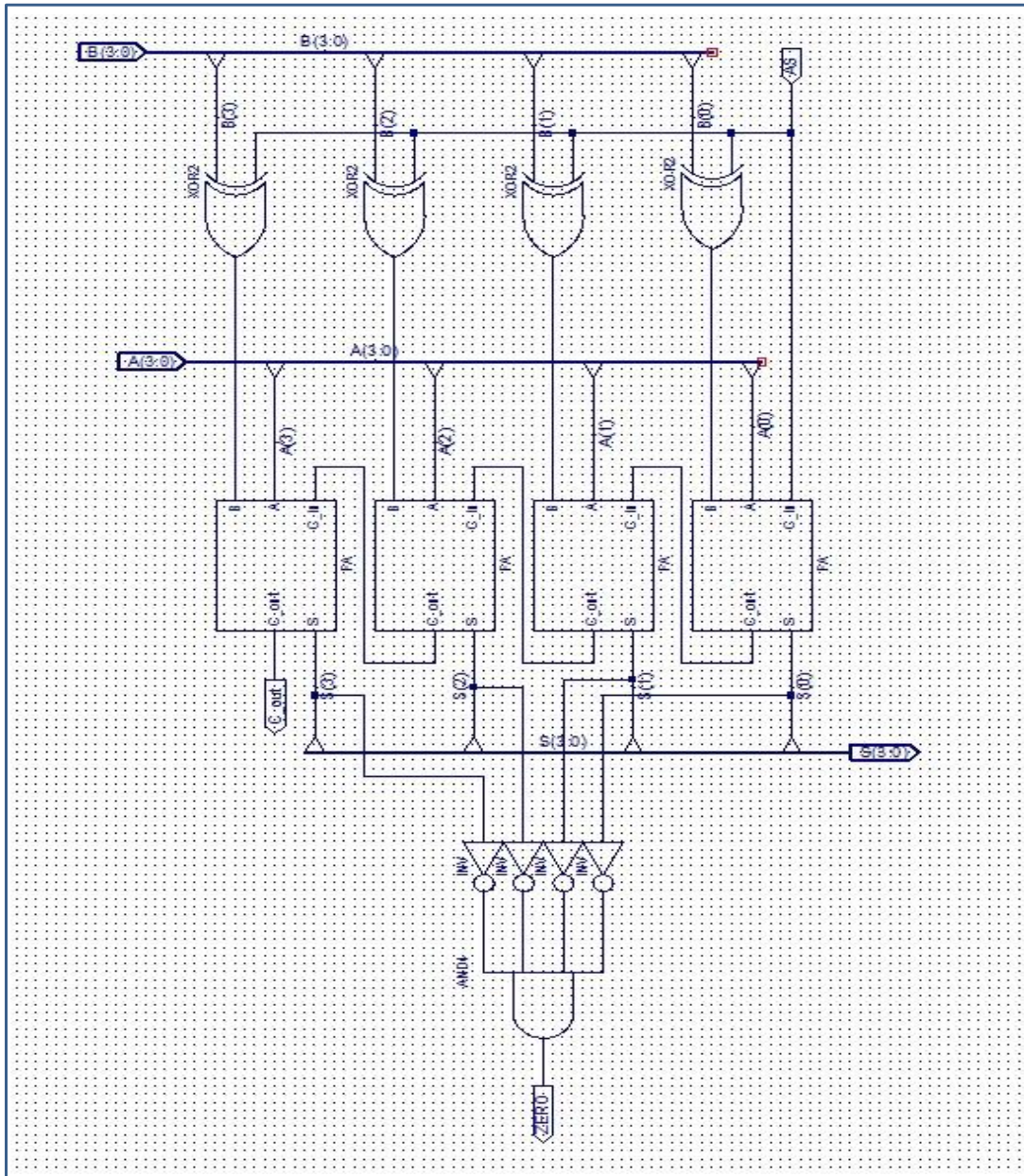

➤ Program counter:

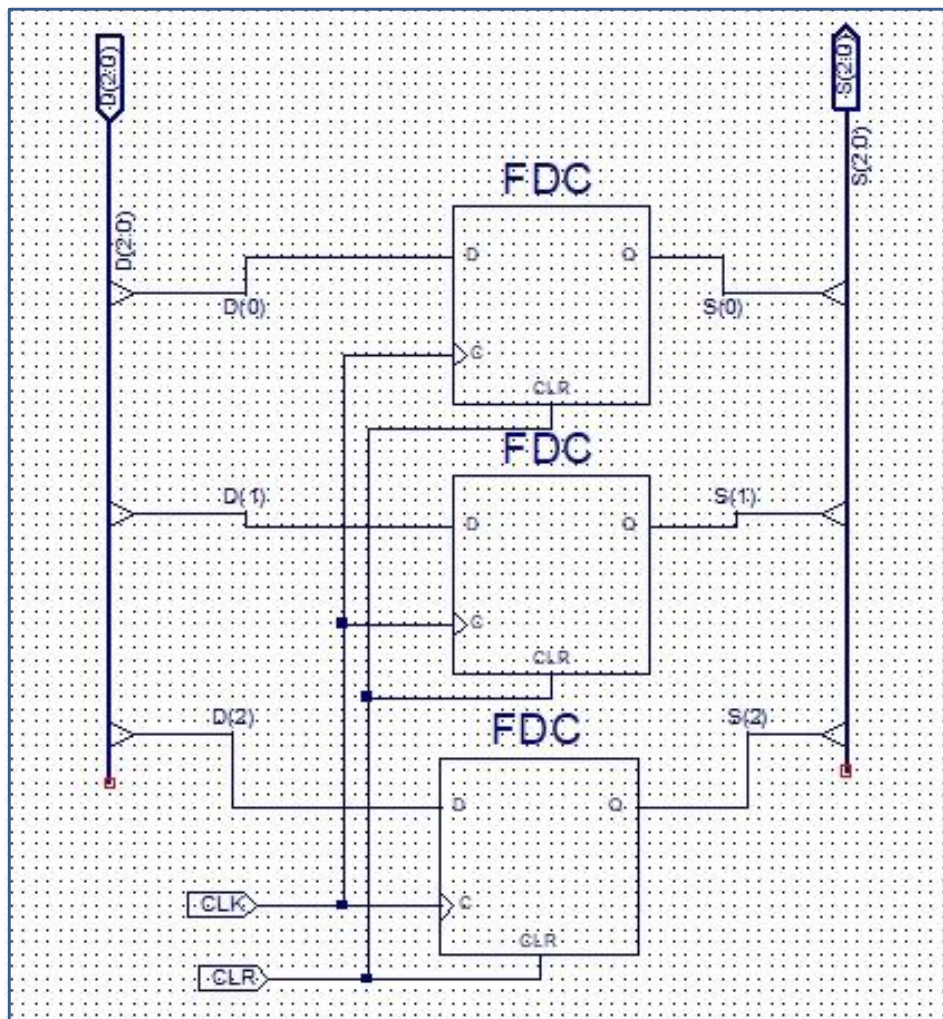


✓ Timing diagram of PC:

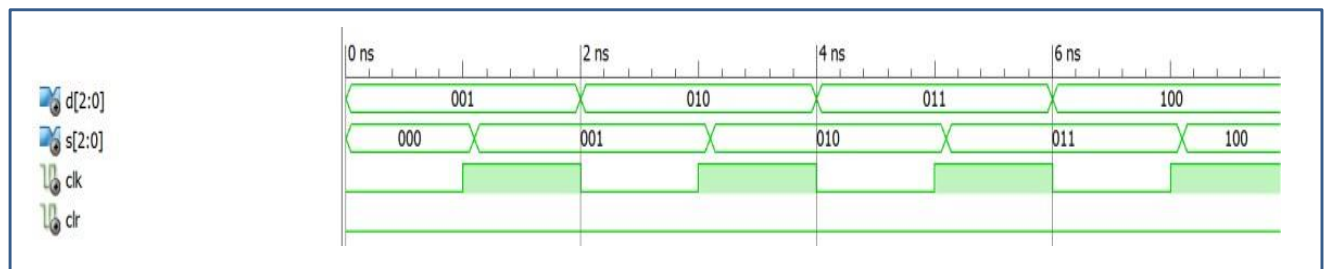


➤ **Register:**

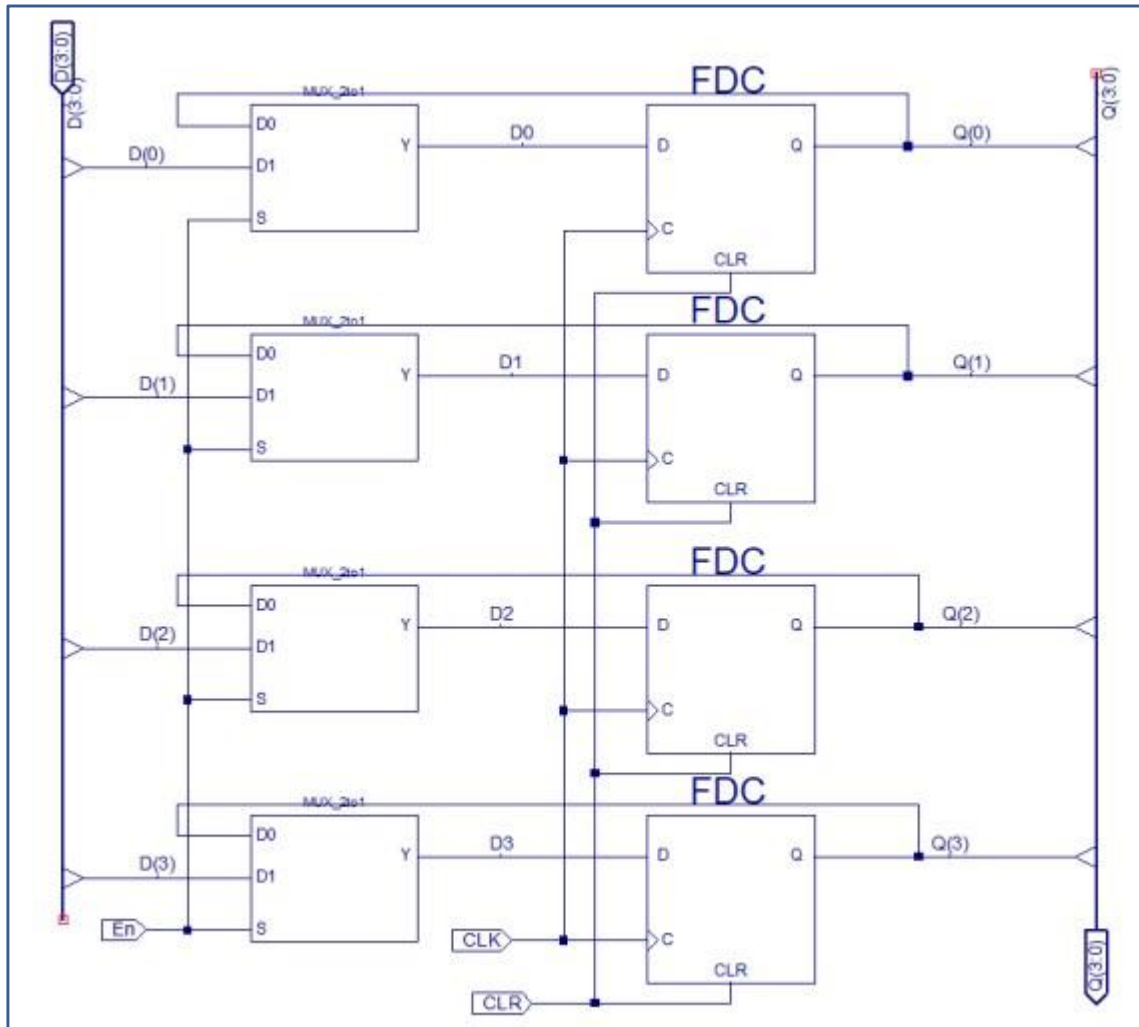Since registers store data, we used D flip-flops to make Register.




➤ Register Bank:

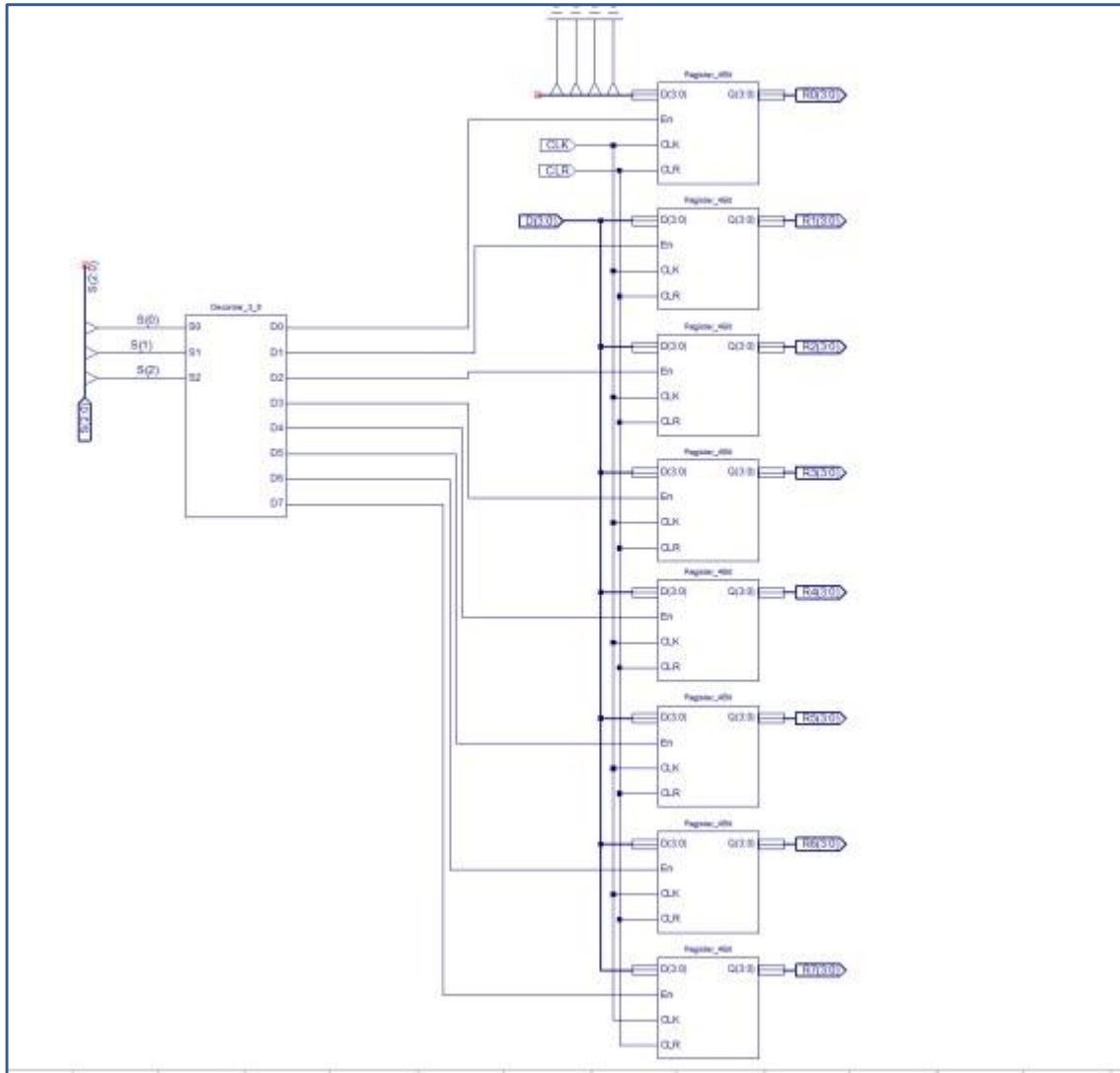
Schematic of Register bank is as follows and we created a symbol of Register bank in the name of




➤ Schematic diagram of ROM:

 

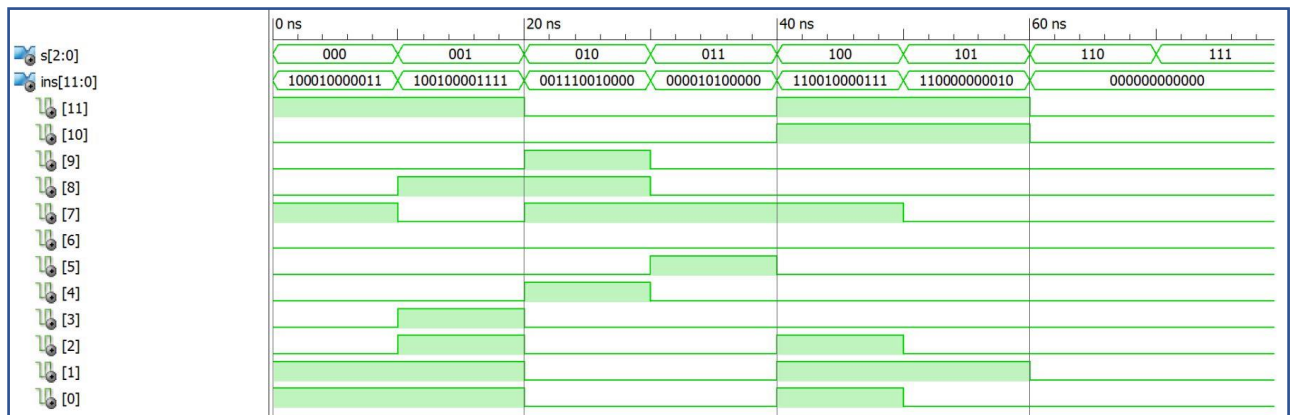
✓ Simulation diagram of Rom is as follows:



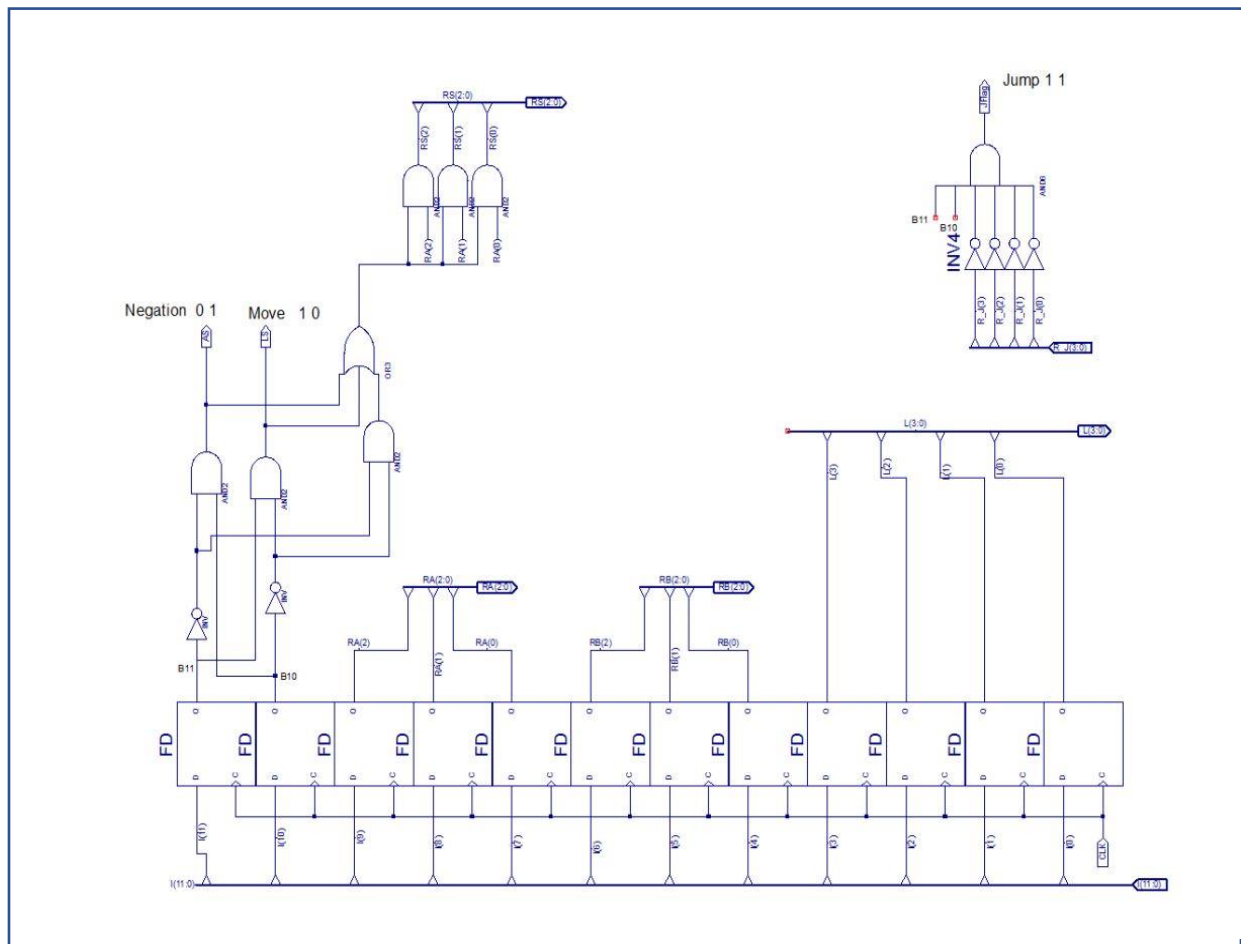➤ Schematic diagram of Instruction decoder is as follows:



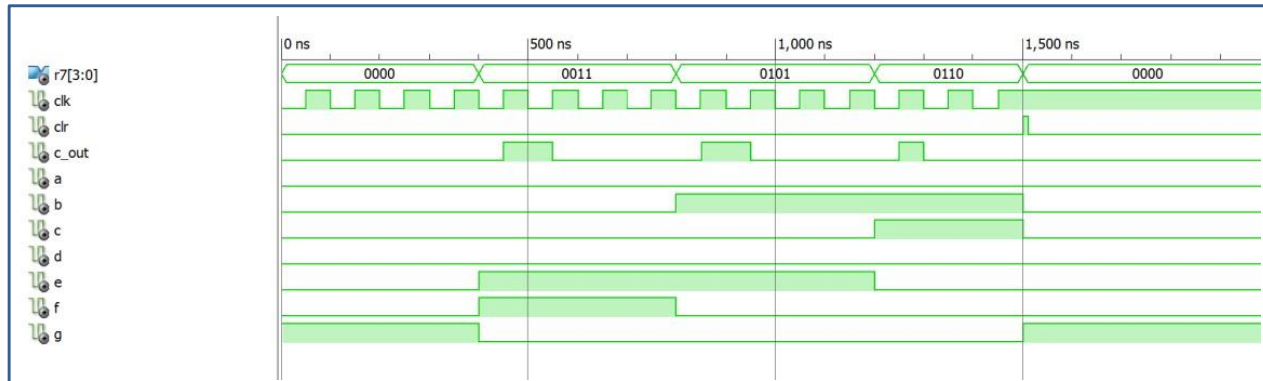- Simulation diagram of Nano-Processor is as follows:



➤ Assembly program and corresponding machine code representation :

	B11	B10	B09	B08	B07	B06	B05	B04	B03	B02	B01	B00
MOVI R1, 3	1	0	0	0	1	0	0	0	0	0	1	1
MOVI R2, -1	1	0	0	1	0	0	0	0	1	1	1	1
ADD R7, R1	0	0	1	1	1	0	0	1	0	0	0	0
ADD R1,R2	0	0	0	0	1	0	1	0	0	0	0	0
JZR R1, 111	1	1	0	0	1	0	0	0	0	1	1	1
JZR R0, 010	1	1	0	0	0	0	0	0	0	0	1	0
	0033	0030	0004	0006	001D	0000	0008	0004	0002	0012	0033	0013

➤ Discussion:

Initially we used the default clock in BASYS which is about 50MHz. But with this clock rate we are unable to demonstrate the changes in the 7-segment display. Hence, we used a 'slowdown' mechanism using RCA and some other logics (especially the D-flip flops). We have slowed down the clock by sixteen times(X16) by a single slow down unit. Here we used 5 such units leading a 2^{20} slow down and managed to get a visible change in seven segment display.

Conclusions from the lab:

- Simple Nano processor can be developed using ISE design suite.
- Hierarchical design is very important design technique to make complex designs.
- Instructions decoders can be developed using basic logic gates and some proper logic.
- Instruction decoders are the vital part of processor design.
- Instruction decoders are the one which decode the machine code and activate necessary components to execute the instruction.
- The amount of data can be handle by a processor is determined by register size.
- Much instructions can be fetched into processor by increasing instruction memory.
- Instruction execution can be speed up by activating them on both edges of a pulse.
- The action of program counter, the loading of instructions from ROM, decoding and activating necessary registers to load values, performing add/sub function and reloading them to registers have been studied and practical experience on how they work have been gained.

✓ Team Coordination:

Index number	Works Assigned	Time taken
160544C	Register, Instruction Decoder, Final Assembling, slow_down mechanism	6 hours
160400H	Program Counter, ROM, Register bank Worked on Look-up table, Final Assembling	5 hours
160658E	Basic Adders, All Multiplexers, Add/Sub unit, Worked on Look-up table, Final Assembling	5 hours